

Designing a flyback DC/DC converter

Video 2

Fundamentals of flyback converters

Brigitte Hauke – Boost and Buck-Boost Controller Application Manager


Youhao Xi – Boost and Buck-Boost Controller Application Manager

February 2023

Outline of video series




1. Guidelines for topology selection
2. Fundamentals of flyback converters
3. Flyback converter design procedure I
4. Flyback converter design procedure II
5. Flyback transformer basics
6. Practical issues experienced with flyback converters

Flyback topology derivation

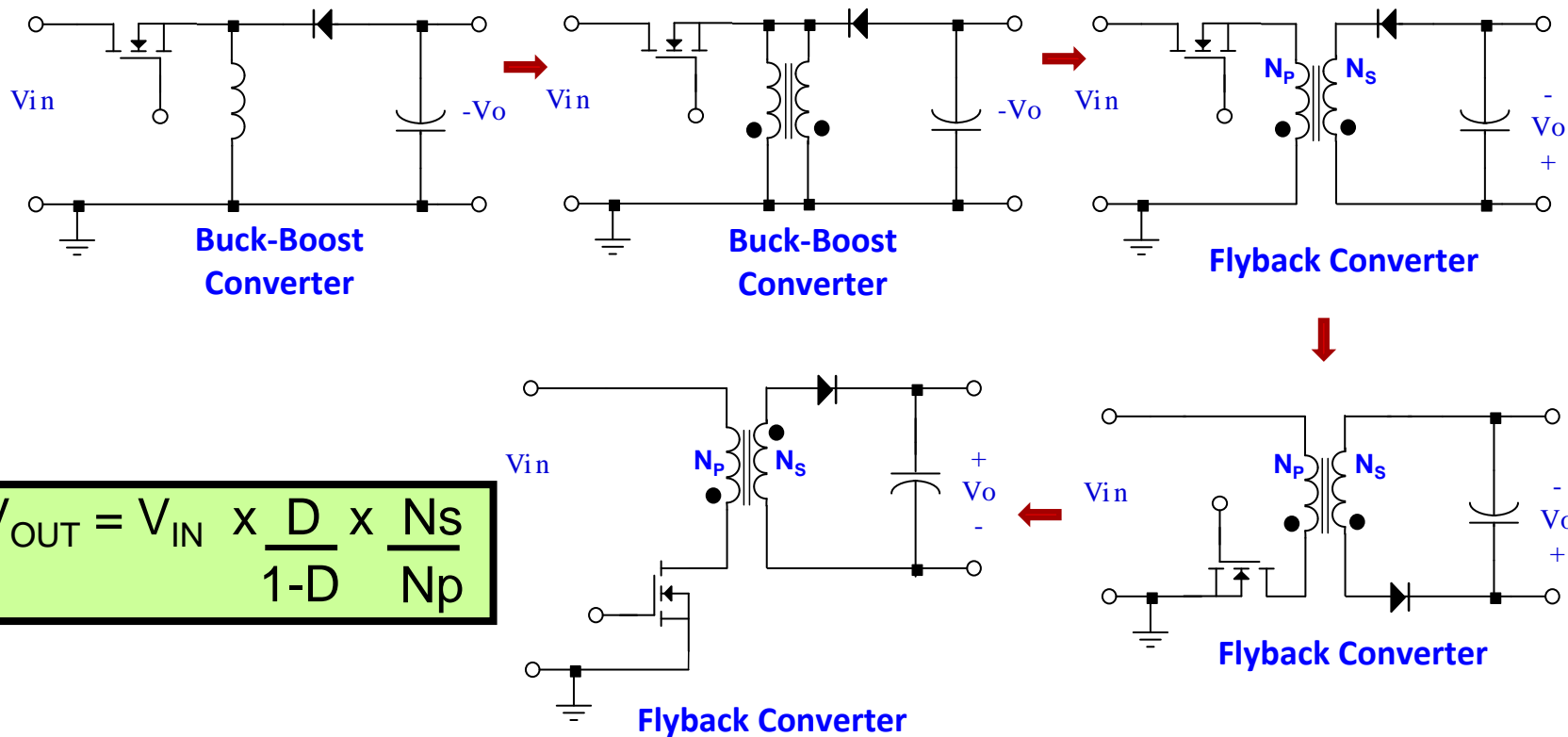


Operating principle

- Key Waveforms

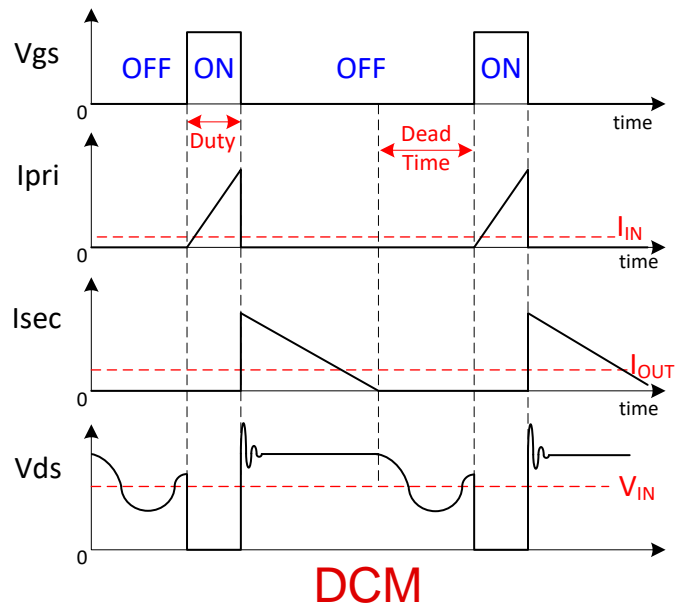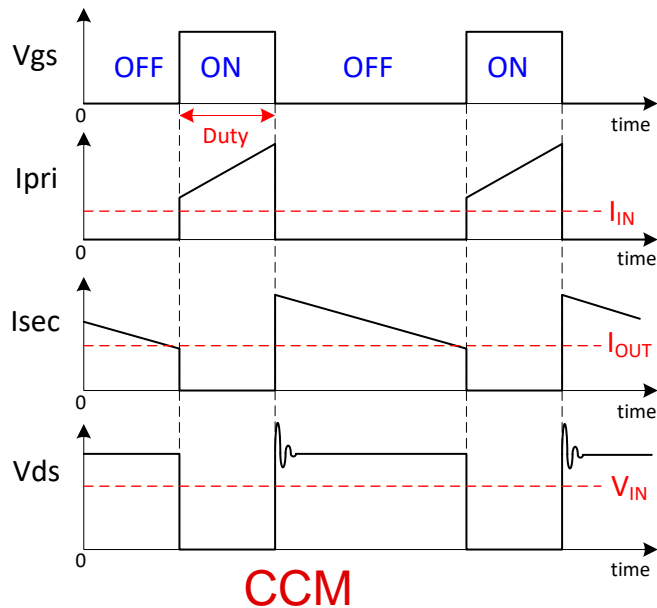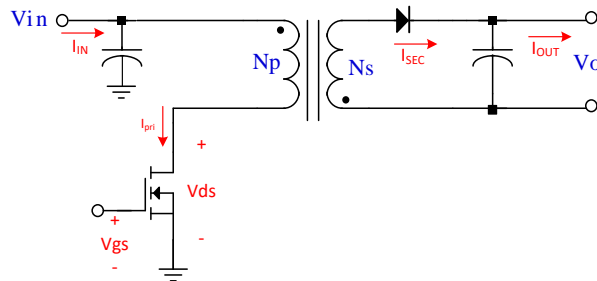


Operating principle

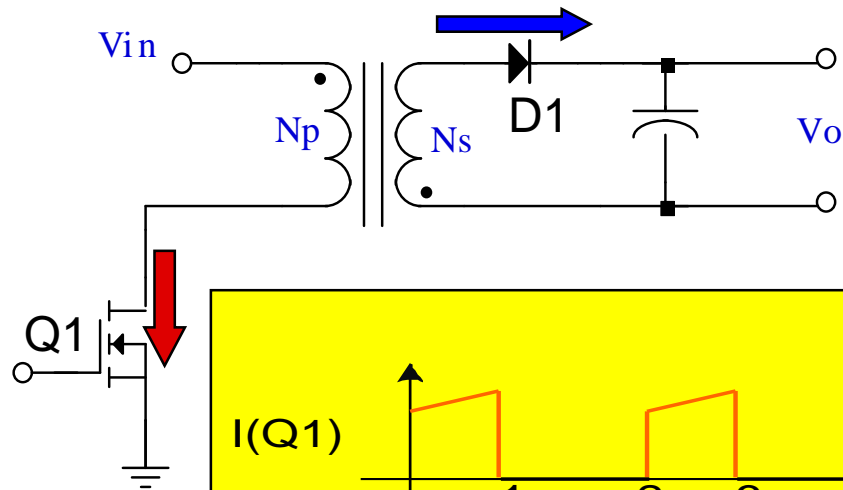

Continuous Conduction Mode
Input/Output relationship:
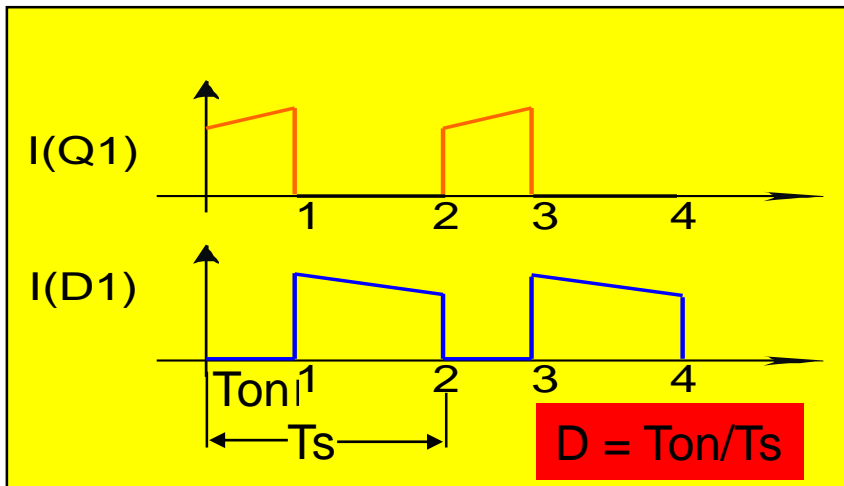
$$V_{OUT} = V_{IN} \times \frac{D}{1-D} \times \frac{N_s}{N_p}$$



Steady state analysis

Duty Cycle:
$$D = \frac{V_{OUT} + V_F}{V_{OUT} + V_F + \frac{N_s}{N_p} \cdot V_{IN}}$$

Primary Circuit:

Average:
$$I_{avg} = \frac{P_{OUT}}{V_{IN} \cdot \eta}$$



Peak:
$$I_{pk} = \frac{1}{2} \cdot \frac{V_{IN}}{L_m} \cdot \frac{D}{f_{SW}} + \frac{I_{avg}}{D}$$

RMS:
$$I_{rms} = \frac{I_{avg}}{\sqrt{D}}$$

Ripple:
$$I_{AC} = \sqrt{I_{rms}^2 - I_{avg}^2}$$

$$= I_{avg} \cdot \sqrt{\frac{1-D}{D}}$$

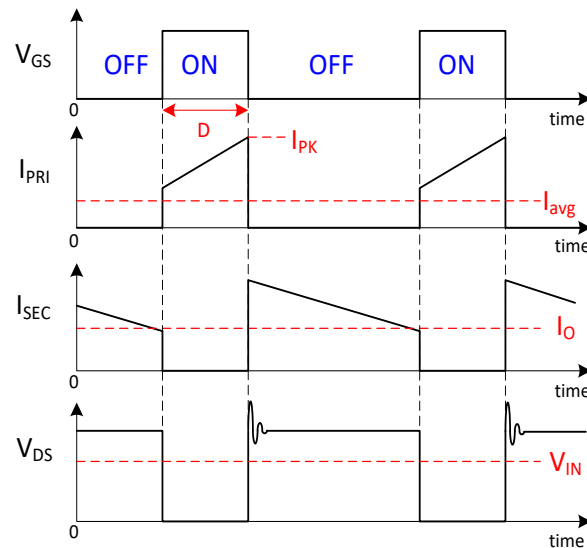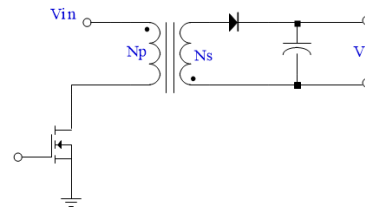V_{DS} :
$$V_{DS} = V_{IN} + \frac{N_p}{N_s} \cdot (V_{OUT} + V_F)$$



Steady state analysis

Secondary Circuit:

Avg:



$$I_{OUT}$$

Ripple:

$$I_{ac_sec} = I_{OUT} \cdot \sqrt{\frac{D}{1-D}}$$

PIV:

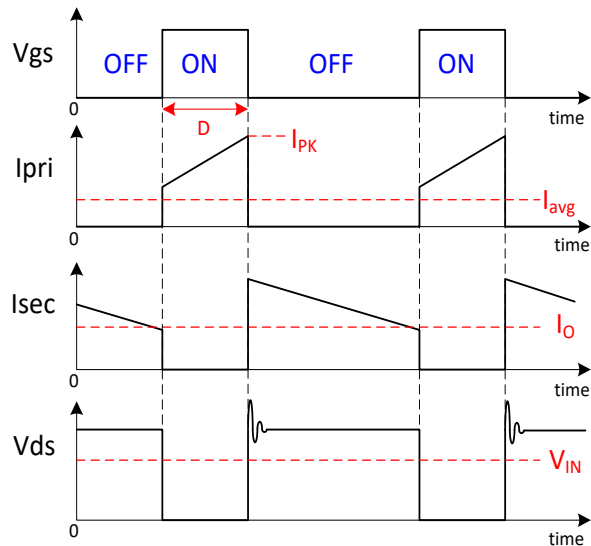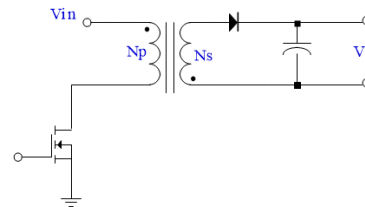
$$V_r = V_{OUT} + \frac{N_s}{N_p} V_{IN}$$



Flyback RHPZ

- The Right Half Plan Zero (RHPZ) affects the speed of dynamic response
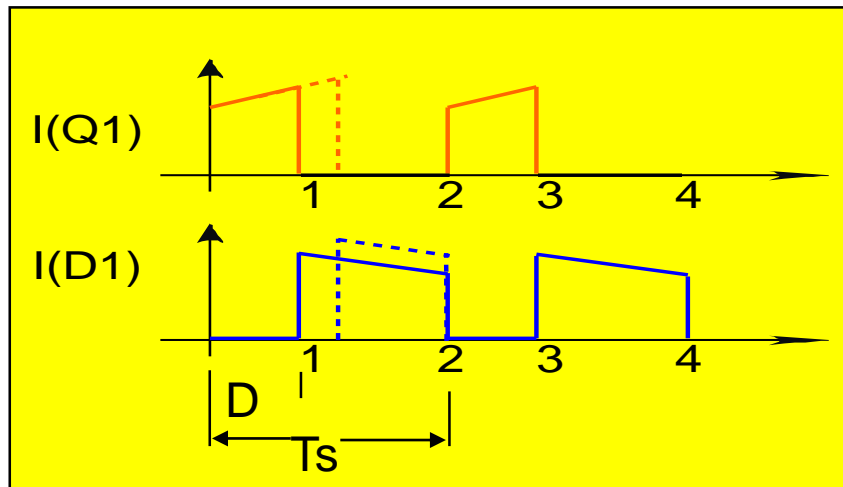
$$F_{\text{RHPZ}} = \frac{V_{out} \cdot (1-D)^2}{2 \cdot \pi \cdot D \cdot L_s \cdot I_{out}}$$



Details on RHPZ: <https://www.ti.com/seclit/ml/slup084/slup084.pdf>

Video 1 and 2 Summary – Video 3 to 6 Outlook

- **We discussed**
 - **Topology selection guidelines** based on power level
 - Flyback and sepic topologies comparison and their suitable applications
 - **Fundamentals of flyback:** operating modes and key parameters
- **We will discuss**
 - **Design procedure** demonstrated with LM5155 example, **for non-isolated, PSR and isolated applications**
 - **Flyback transformer basics**, and the need of air gap
 - **Frequently asked questions** including multi rails, light load regulation, and high input voltage solutions, and **commonly seen mistakes**

Tools and application collaterals

Most important: E2E Forum <https://e2e.ti.com/support/>

All the following are available in the product folders on <https://www.ti.com/>

1. Flyback EVMs and user's guides
2. Excel design calculators
3. WEBENCH™ Power Designer support
4. PSpice® models
 - Transient model supports flyback
 - We are adding more average models for flyback loop simulation
5. Application notes
6. Reference designs
 - You can find many flyback reference designs at:
<https://www.ti.com/reference-designs/index.html>



© Copyright 2023 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)